

A Ten-Decade Logarithmic Current-to-Voltage Converter

The DN120 logarithmic I/V converter is capable of translating the entire dynamic range of current (10 fA–100 μ A) produced by various sensors into a buffered output voltage that can easily be measured and recorded by a data acquisition system.

Jim Phalan, Dawn Electronics Inc.

Logarithmic current-to-voltage (I/V) converters are called for when current over a large dynamic range is to be measured without the use of gain adjustment. Until recently, converters could operate only over a six-decade dynamic range (1 nA–1 mA) of input current. Sensors such as photodiodes, ionization chambers, and photomultipliers, however, often have current outputs far below 1 nA.

Theory

The DN120 logarithmic I/V converter is capable of measuring current from ± 10 fA to ± 100 μ A. The input stage of this device (see Figure 1, page 52) is a transimpedance amplifier consisting of a pnp and an npn low-leakage silicon transistor and an ultra low current op amp. The output voltage V_A comes from the idealized intrinsic transistor equation for silicon [1]:

$$V_{BE} = \frac{kT}{q} \ln \left[\frac{I_C + I_B}{I_S} + 1 \right] = -V_A \quad (1)$$

where:

- $I_C = I_{IN}$, if $I_{IN} \gg I_B$
- V_{BE} = base-to-emitter voltage of conducting transistor
- I_C = forward collector current of transistor
- I_S = reverse saturation current of transistor

k = Boltzmann's constant (1.38×10^{-23} joules/kelvin)

T = absolute temperature in kelvin

q = unit electron charge (1.6×10^{-19} coulomb)

This equation shows that the conducting transistor's base-to-emitter voltage is proportional to the natural logarithm of the collector current. If the op amp leakage current I_B is small compared to the input current, the amplifier output voltage V_A is proportional to the logarithm of the input current I_{IN} . This fundamental property of a transistor is used in almost all logarithmic I/V converters.

Although it is not apparent from Equation 1, temperature has a strong influence on diode characteristics. The reverse saturation I_S roughly doubles with every 10°C increase in junction temperature [2]. As a result, the temperature coefficient of V_{BE} is approximately -2 mV/°C. Conventional logarithmic I/V converters use temperature compensation

techniques to reduce this effect, but these devices are generally limited to a six-decade dynamic range.

The DN120 differs from other logarithmic converters in that the diodes are mounted on a thermoelectric cooler stabilized to 23°C (296.2 kelvin) to prevent ambient temperature variations from affecting the diode characteristics. The equation relating the output voltage V_A to the input current I_{IN} for the amplifier in Figure 1 is then:

$$V_A = -25.5 \cdot 10^{-3} \ln \frac{I_{IN}}{I_S} \quad (2)$$

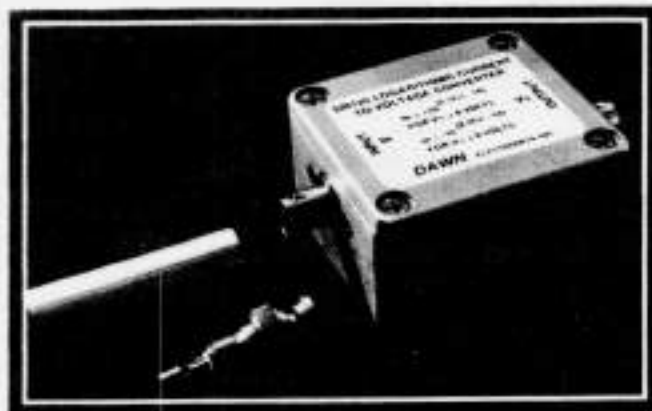


Photo 1. The current-to-voltage converter's dynamic range was tested on a radiometer. Shown here before final assembly, the equipment consisted in part of the converter, the cylinder (left of the converter) that kept direct sunlight from striking the photodiode, and the photodiode (below the cylinder).

Tri-Axial Accelerometers

Precision Aligned

Less than 0.5° deviation from ideal
Less than 0.25% transverse sensitivity

Built-in Signal Conditioning

Wide Temperature Range

A force-balanced design minimizes variations due to temperature and aging effects, resulting in a sensor that is more stable over temperature than piezoelectric or piezoresistive devices.

Built-in Custom Filtering

Small Size

Single +5 Volt Supply

Rugged

Will survive 500 g powered.



New
Low-G
Ranges!

34103A

DC-coupled Ranges

±1, ±1.5, ±2, ±2.5, ±3, ±5, ±7.5 g
and custom



New
Ranges!

34100A

DC-coupled Ranges

±10, ±15, ±20, ±25, ±30, ±50, ±75 g
and custom

Call or FAX today!

(330) 659-3312

FAX: (330) 659-3286

www.summitinstruments.com



Summit Instruments, Inc.
2236 N. Cleveland-Massillon Rd
Akron, Ohio 44333-1255 USA

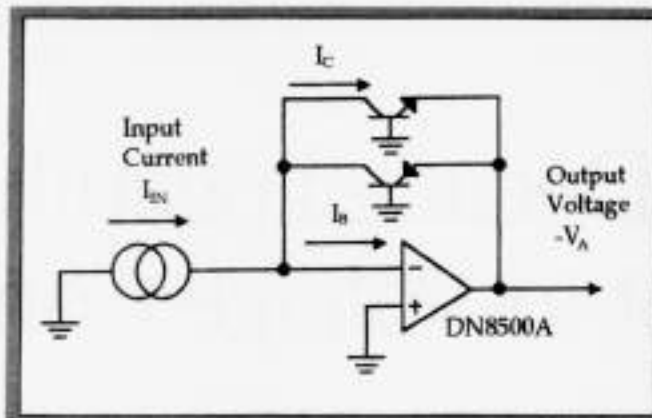


Figure 1. The transistor-lens amplifier in the first stage of the DN120 produces an output voltage that is the logarithm of the input current.

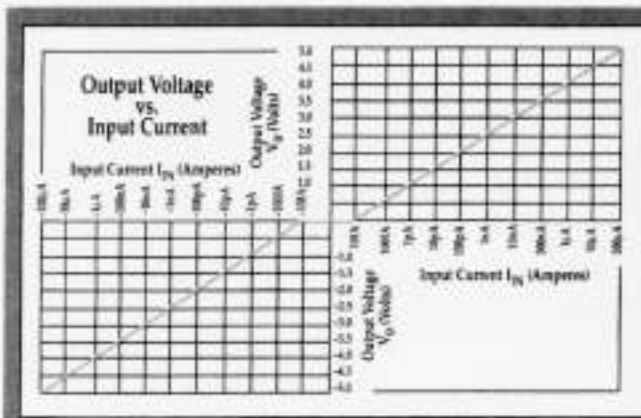


Figure 2. The output voltage of the DN120 is zero when the input current is greater than -10 fA and less than +10 fA.

where:

$$I_{IN} = I_C \text{ and } I_{IN} / I_S \gg 1$$

And the change in output voltage per decade change in input current is:

$$V_{A2} - V_{A1} = -25.5 \cdot 10^{-3} \ln \frac{I_{IN2}}{I_{IN1}} \quad (3)$$

$$= -58.8 \text{ mV}$$

for $I_{IN2} = 10 \cdot I_{IN1}$

The smallest current the converter can measure is determined by the reverse saturation current I_S of the transistors and the input leakage current of the op amp. The reverse saturation current I_S is <0.5 fA at 25°C for the DN120's transistors and the input leakage current of the DN8500A, an ultra low current op amp available from Dawn Electronics, is typically <2 fA. The low reverse saturation current of the transistors and low input current of the op amp enable the converter to measure input current down to 10 fA and to resolve current changes of <1 fA.

Circuit Design

The DN120 was designed to produce an output voltage that increases 0.5 V/decade change of input current, and to deliver ±5.0 V when the input current is ±100 μA

(see Figure 2). When the input current is positive, transistor Q1 conducts; when it is negative, Q2 conducts. The output voltage V_A from this stage, which increases 58.8 mV/decade, is fed into two active rectifier circuits that have independent full-scale and gain adjustments for positive and negative input current (see Figure 3, page 53). Recombining these signals produces the output voltage. Equations 4.1 through 4.4 define the converter's I/O characteristics:

| Positive Input Current | Negative Input Current |
|---|---|
| (4.1) $V_O = +10 \cdot (V_O)^{-10}$ For $5 \text{ V} > V_O > 0$ | (4.3) $V_O = -10 \cdot (V_O)^{-10}$ For $-5 \text{ V} < V_O < 0$ |
| (4.2) $V_O = + \left[7 \cdot \frac{\text{Log} I_{IN} }{2} \right]$ For $10^{-4} > I_{IN} > 10^{-14} \text{ A}$ | (4.4) $V_O = - \left[7 \cdot \frac{\text{Log} I_{IN} }{2} \right]$ For $-10^{-4} < I_{IN} < -10^{-14} \text{ A}$ |

Application

A simple radiometer incorporating a 1.2 mm² silicon photodiode from Centronic Inc. (Newbury Park, California) was constructed to demonstrate the converter's dynamic range (see Photo 1, page 51). The photodiode was connected to the input of the DN120 as shown in Figure 4 (page 53). Photodiode current I_{IN} , which is directly proportional to the incoming radiation, flows

NEW TRANSDUCER SOLUTIONS FROM ITC...

ITC announces the addition of three new lines of ultrasonic transducers to solve your sensor design problems.


ITC 9080 SERIES



9081 92 kHz
9082 150 kHz
9083 215 kHz

Our new ITC 9080 series of teflon encased transducers are perfect for demanding environments.

ITC 9090 SERIES

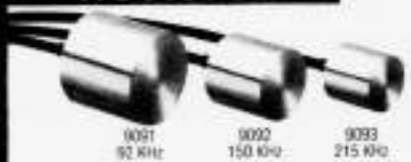

9091 92 kHz
9092 150 kHz
9093 215 kHz

The new ITC 9090 series features a 316 stainless case suitable for food and chemical processing applications.

ITC 9070 SERIES



9071 92 kHz
9072 150 kHz
9073 215 kHz

The ITC 9070 series is still the choice for low cost and high reliability, with enhanced acoustic performance.

ITC 9070-1/-2



The new ITC 9070-1/-2 is a 4.5 MHz transducer pair good for contact measurement; close range, high-res proximity sensing; and bubble detection.

Call us today with your problems.

We have the solution...

ITC

International Transducer Corporation

For more information call our sales office at (805) 663-2575 ext. 521
869 Ward Drive
Santa Barbara, California 93111
Fax (805) 967-8199
Now on the web at: www.itc-transducers.com

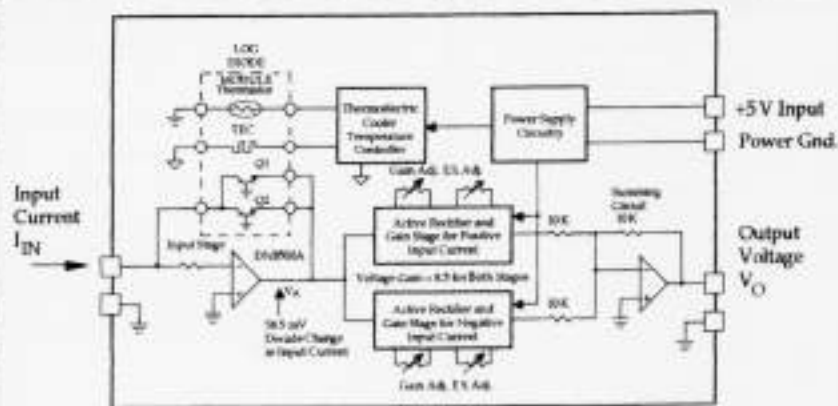


Figure 3. The two different signal paths for positive and negative input current are necessary to ensure that the output voltage goes to zero when the input current is between $-10 \mu\text{A}$ and $+10 \mu\text{A}$, and to compensate for slight differences in diode characteristics.

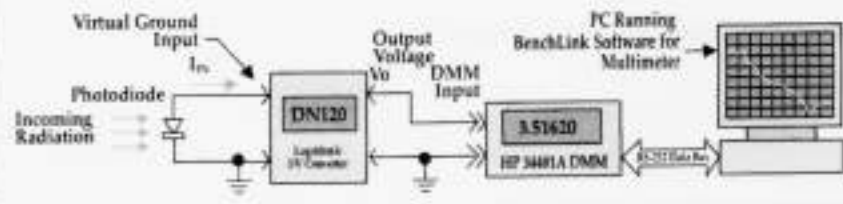


Figure 4. A data acquisition system was used to measure the logarithm of the photodiode current (light intensity) in the radiometer experiment.

into the converter's virtual ground input. This produces an output voltage V_O that is proportional to the logarithm of the current (Equation 4.2).

The radiometer (see Figure 5) was pointed vertically to measure the intensity of the light radiating from the sky. The photodiode was placed in a tube to prevent direct sunlight from entering the aperture. A data acquisition system incorporating a Hewlett-Packard 34401A DMM and a PC running HP34812A BenchLink software measured and recorded the converter's output from 1:16 p.m. to 10:27 a.m. the following day. This time period exposed the photodiode to the maximum radiation of midday and the minimum radiation of early morning. Measurements were made every 30 s. The recorded data were transferred to a Microsoft Excel file.

Figure 6 (page 54) plots the output voltage V_O as a function of time. This voltage is the logarithm of the photodiode current, which can be calculated using Equation 4.1, and is shown on the right Y axis. Note that the DNI20 measured nearly eight decades of photodiode current; the highest light level occurred at the beginning of the test when there were clouds in the radiometer's field of view, and the lowest level in the early morn-

ing hours of the experiment. These extremes occurred at 1:34 p.m. and 2:28 a.m. and produced photodiode currents of $7.08 \mu\text{A}$ and 165 fA respectively.

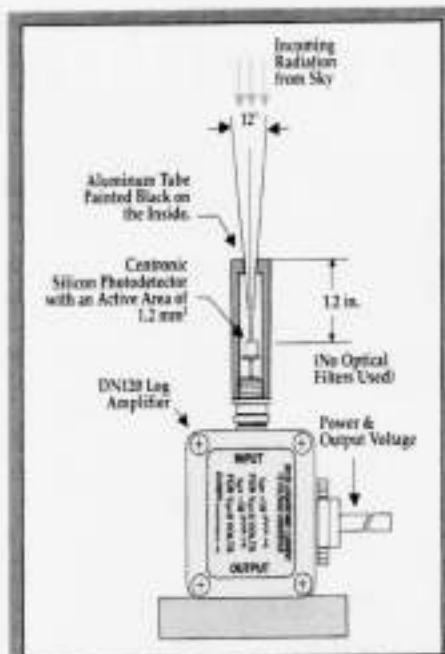


Figure 5. This simple radiometer, using a silicon photodiode, was constructed to demonstrate the dynamic range of the DNI20 logarithmic current-to-voltage converter.

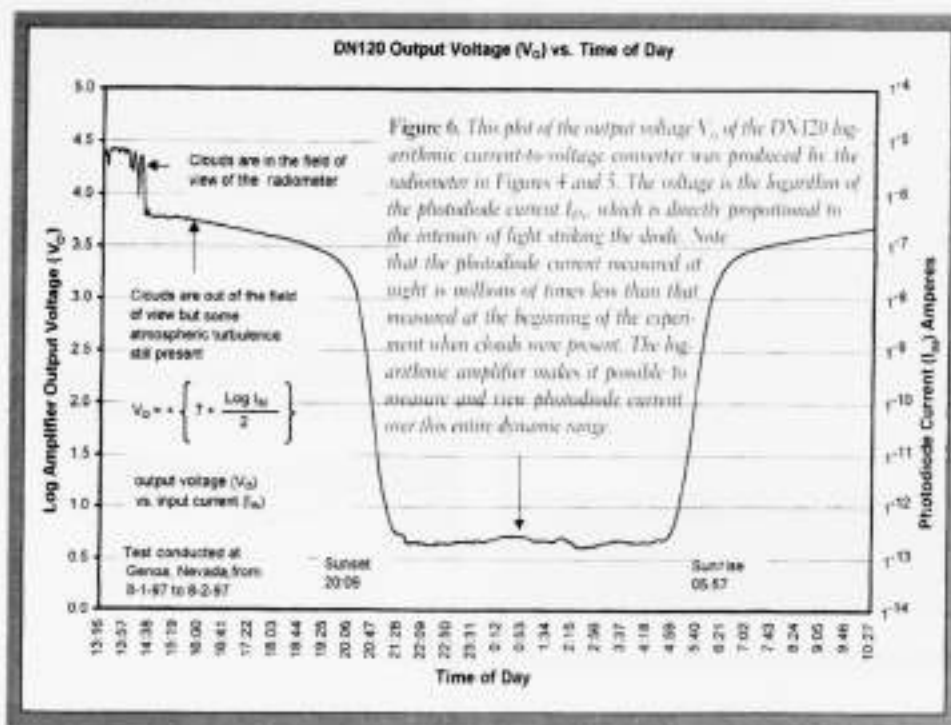


Figure 6. This plot of the output voltage V_o of the DN120 logarithmic current-to-voltage converter was produced by the radiometer in Figures 4 and 5. The voltage is the logarithm of the photodiode current I_{ph} , which is directly proportional to the intensity of light striking the diode. Note that the photodiode current measured at night is millions of times less than that measured at the beginning of the experiment when clouds were present. The logarithmic amplifier makes it possible to measure and view photodiode current over this entire dynamic range.

It must be noted that the radiometer was not calibrated to determine a scale factor between the radiant energy striking the photodiode and the resulting photodiode current. It can be estimated, however, that ~ 6 nA of photodiode current is produced when radiant energy, with flux density of

$1 \mu\text{W}/\text{cm}^2$ (at 900 nm), strikes the Centronic silicon photodiode.

Conclusions

The base-to-emitter vs. collector current relationship of a transistor can be fully exploited in logarithmic I/V converters by

precise temperature stabilization of the log transistor. This is demonstrated by the DN120's 10 decades (33 bits) of logarithmic conversion from 10 EA to 100 μA .

The radiometer application illustrates how almost eight decades of photodiode current were logarithmically converted to usable output voltage. Similar results have been achieved in applications such as ionization chambers used to detect nuclear radiation and photomultipliers that measure ultralow levels of light. ■

References

1. Burr-Brown Linear Products IC Data Book, 1996/97.
2. Motorola Silicon Rectifier Data Manual, Series A, 1980.

Jim Phalan is Director of Engineering, Dawn Electronics Inc., 1004 Mallory Way, Carson City, NV 89701; 702-882-7721, fax 702-882-7675; DawnElect@aol.com or www.dawnelectronics.com

Reader Feedback

To rate this article, circle the appropriate number on the Reader Service Card.

| | | |
|-----------|------|------|
| 7 | 17 | 27 |
| Excellent | Good | Fair |

Just like your LVDT...

solartron
Metrology

...only digital



From the creators of the world's best selling electronic gauging probes comes the Solartron Digital Probe. Just as tough and identical in size, the Digital Probe gives absolute accuracy across the entire measurement range, and multiple probes can be networked to PCs and PLCs (together with Solartron Linear Encoders), or used with our amazing new Digital Readout. Available with spring or pneumatic actuation, there's a Digital Probe to fit your industry. For the complete picture call 1-800-873-5838 today.



solartron Leaders in the art of linear measurement technology

Solartron Metrology, 209 West Second Avenue, Gastonia, NC 28052 www.solartron-metrology.com

ISO9001 CE

DN120 Output Voltage (V_O) vs. Time of Day

